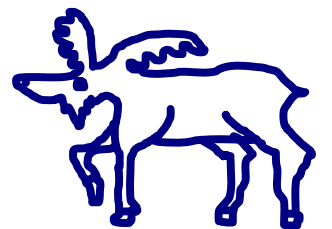


Lecture 15

Pipelined Datapath and Control

Byung-gi Kim

School of Computer Science and Engineering
Soongsil University



4. The Processor

4.1 Introduction

4.2 Logic Design Conventions

4.3 Building a Datapath

4.4 A Simple Implementation Scheme

4.5 An Overview of Pipelining

4.6 Pipelined Datapath and Control

4.7 Data Hazards: Forwarding versus Stalling

4.8 Control Hazards

4.9 Exceptions

4.10 Parallelism and Advanced Instruction-Level
Parallelism


4.11 Real Stuff: the AMD Opteron X4 (Barcelona) Pipeline

Pipelined Version of the Datapath

■ Pipeline register

- ❖ Separation of the two stages
- ❖ Hold information produced in previous cycle

Figure 4.35

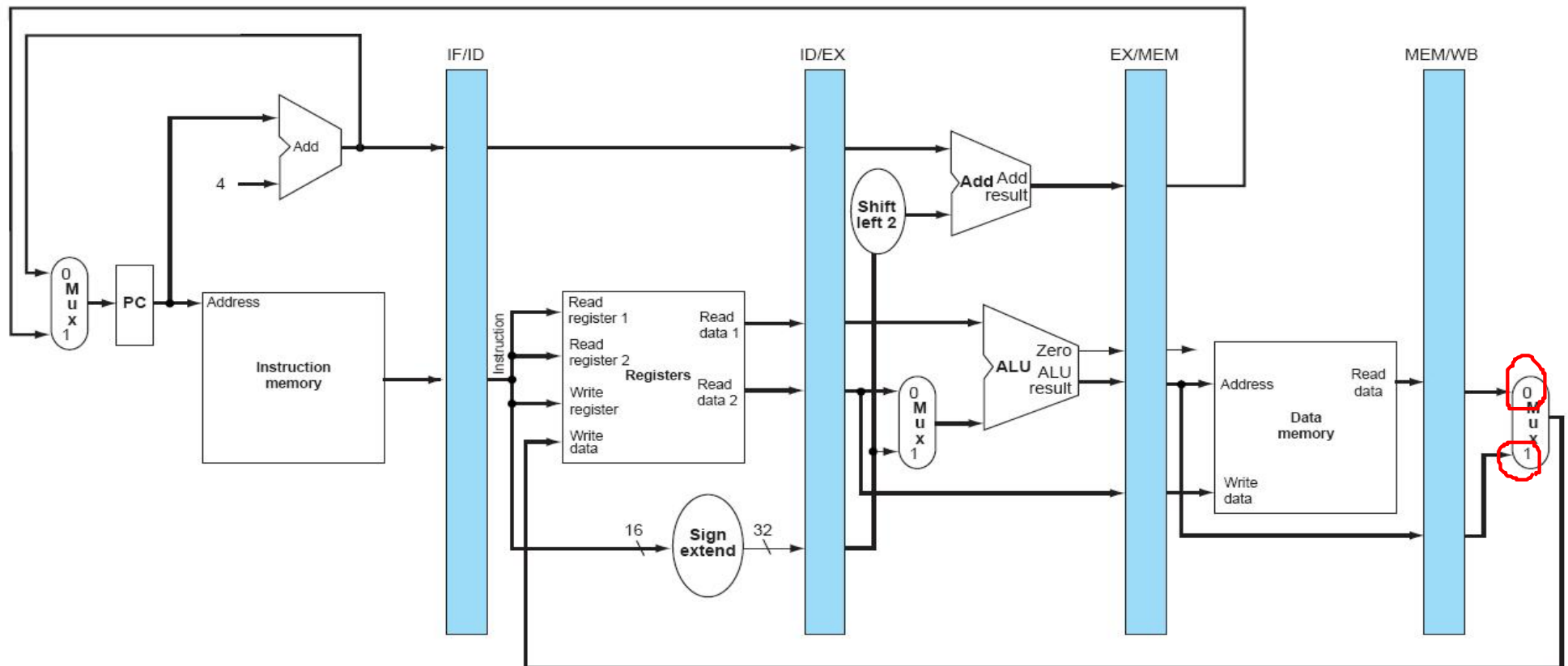

lw Instruction in IF Stage



 


Figure 4.36(a)

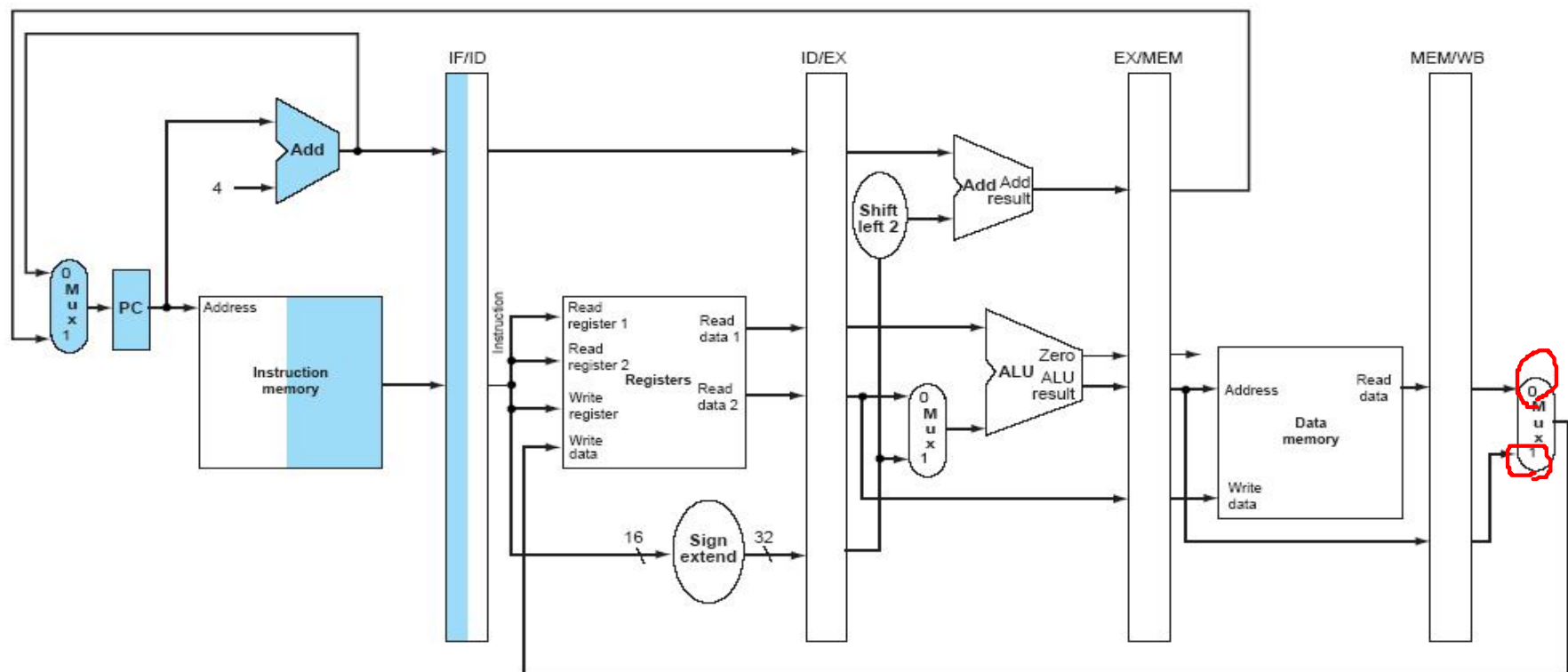

I w Instruction in ID Stage

Figure 4.36(b)

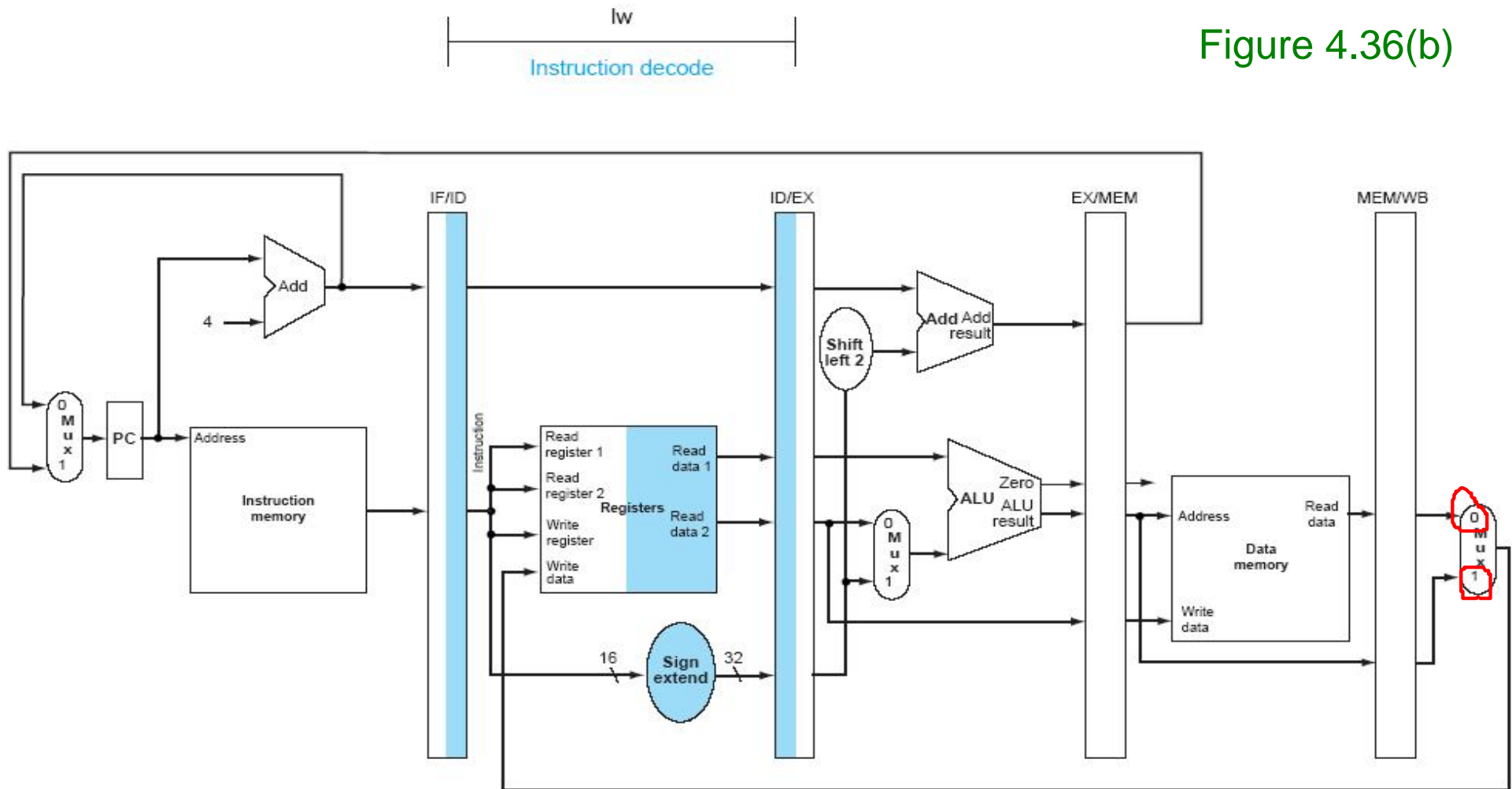

lw Instruction in EX Stage

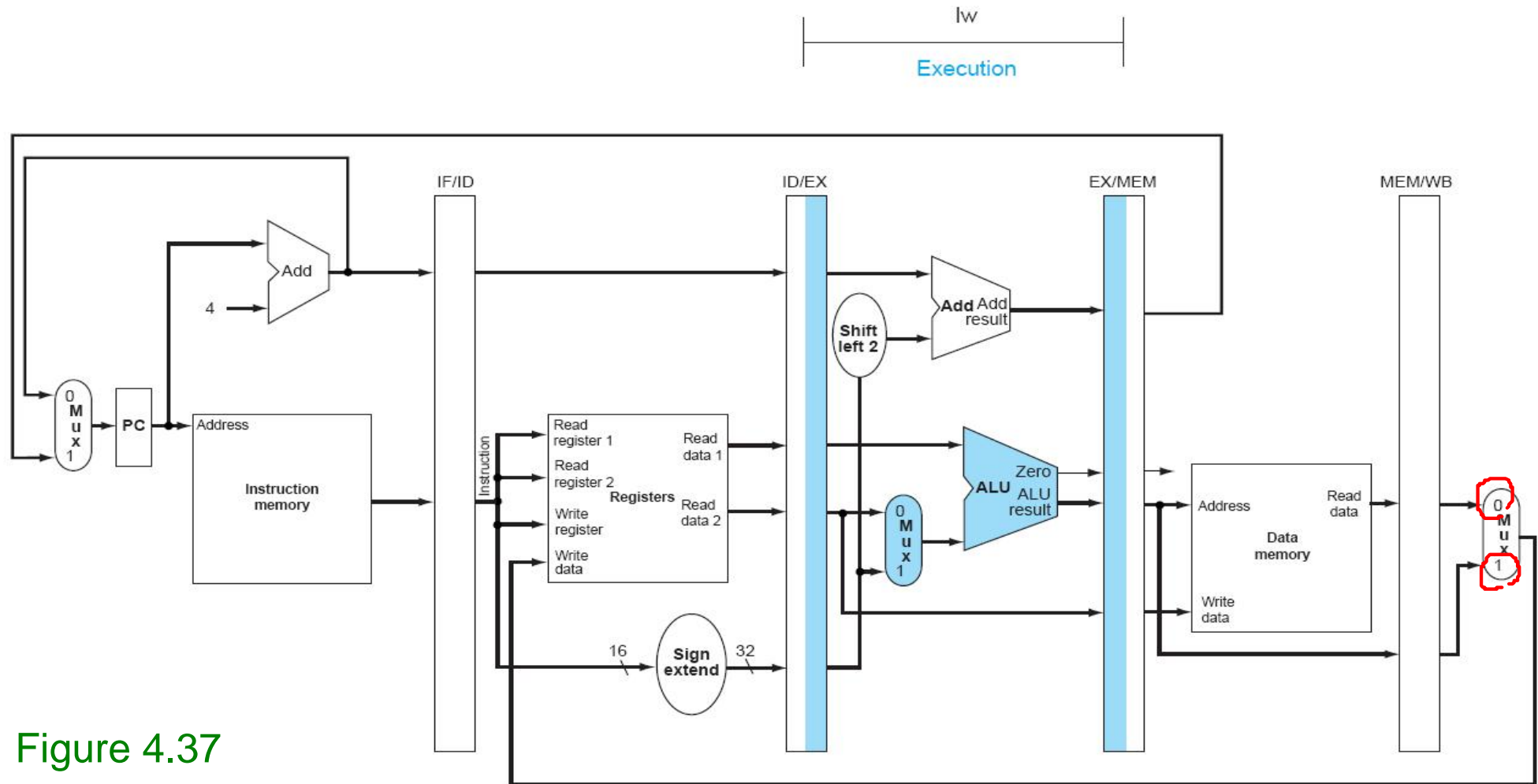


Figure 4.37

lw Instruction in MEM Stage

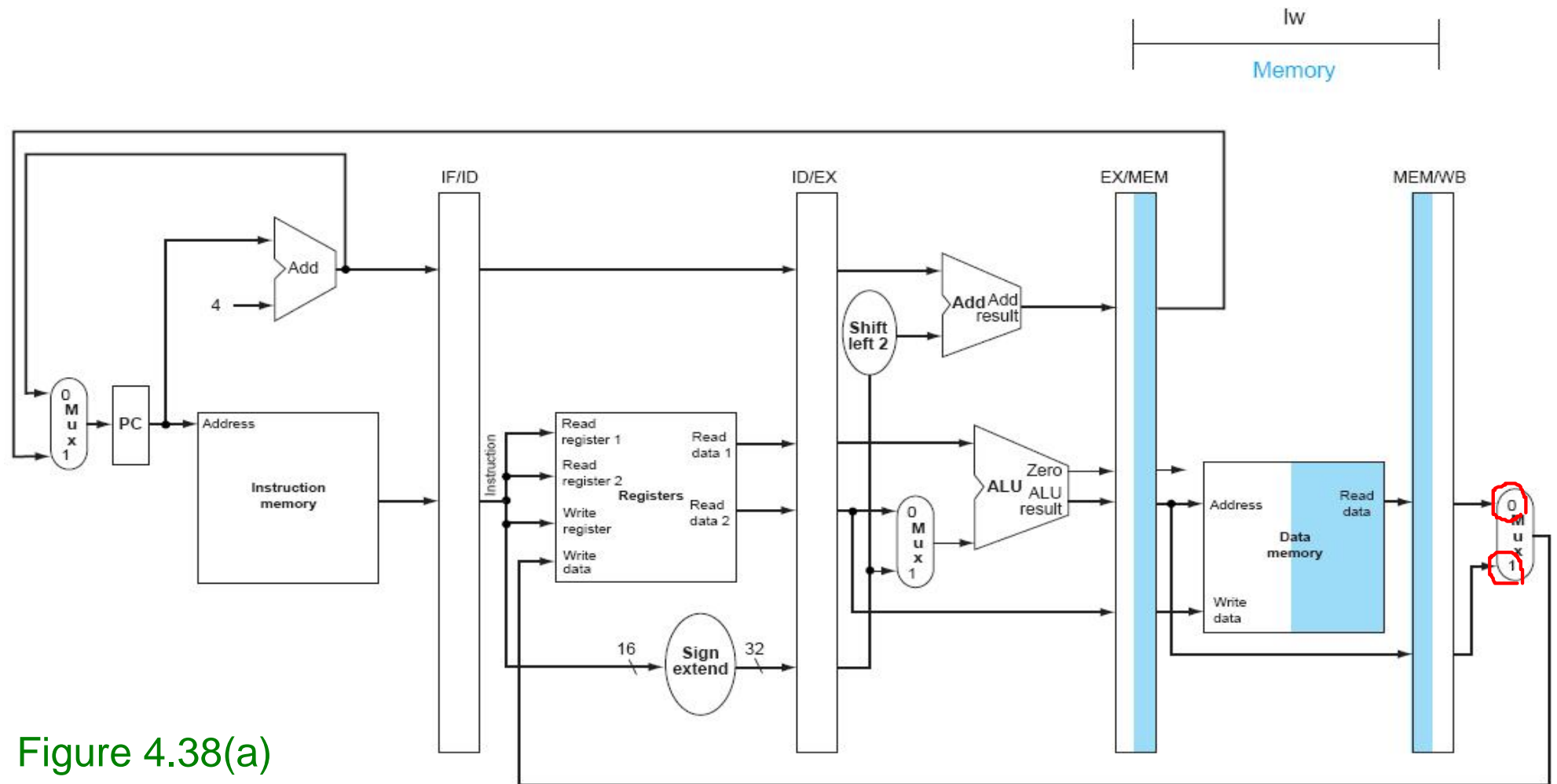


Figure 4.38(a)

lw Instruction in WB Stage

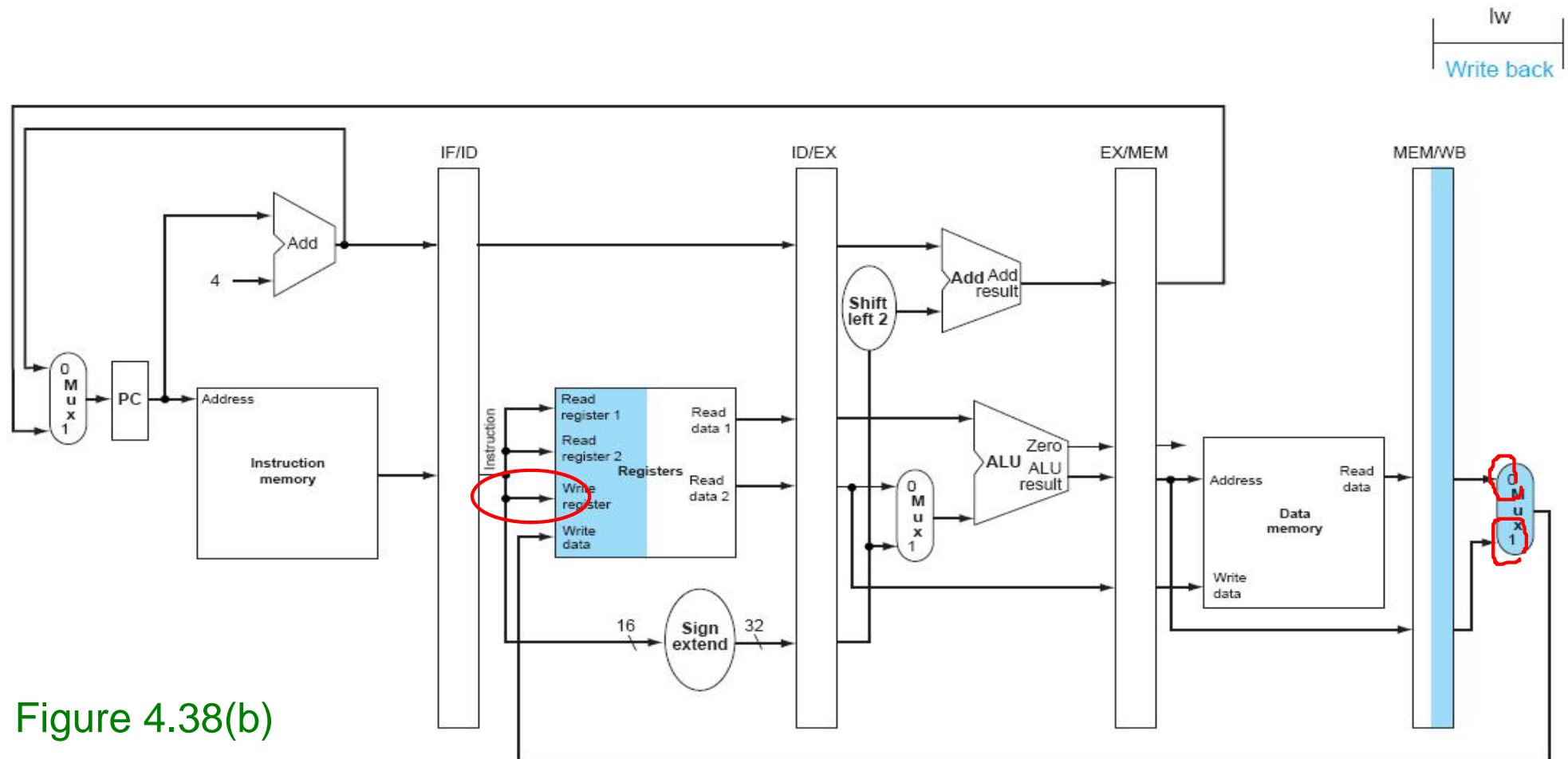


Figure 4.38(b)

Corrected Pipelined Datapath

■ load instruction

- ❖ Write register number: Should be preserved until WB stage

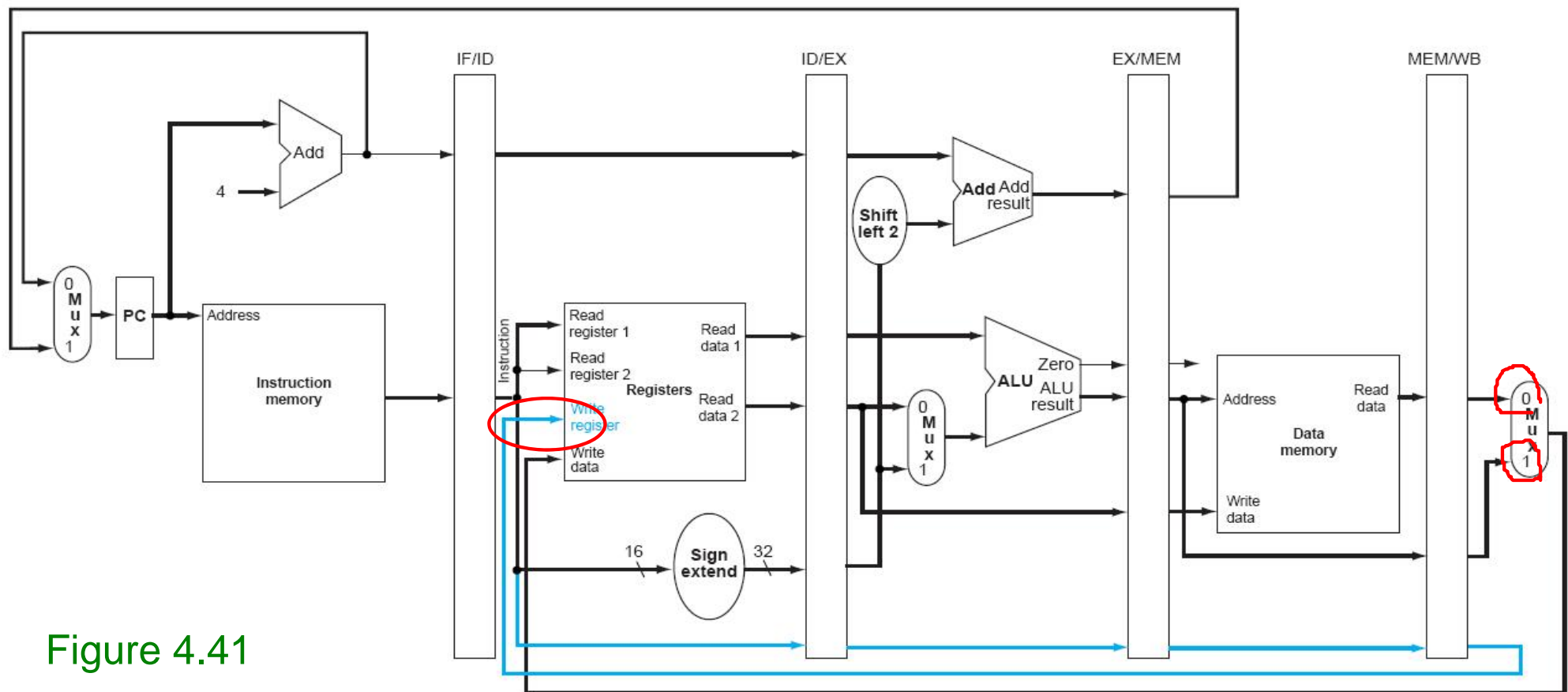


Figure 4.41

sw Instruction in EX Stage

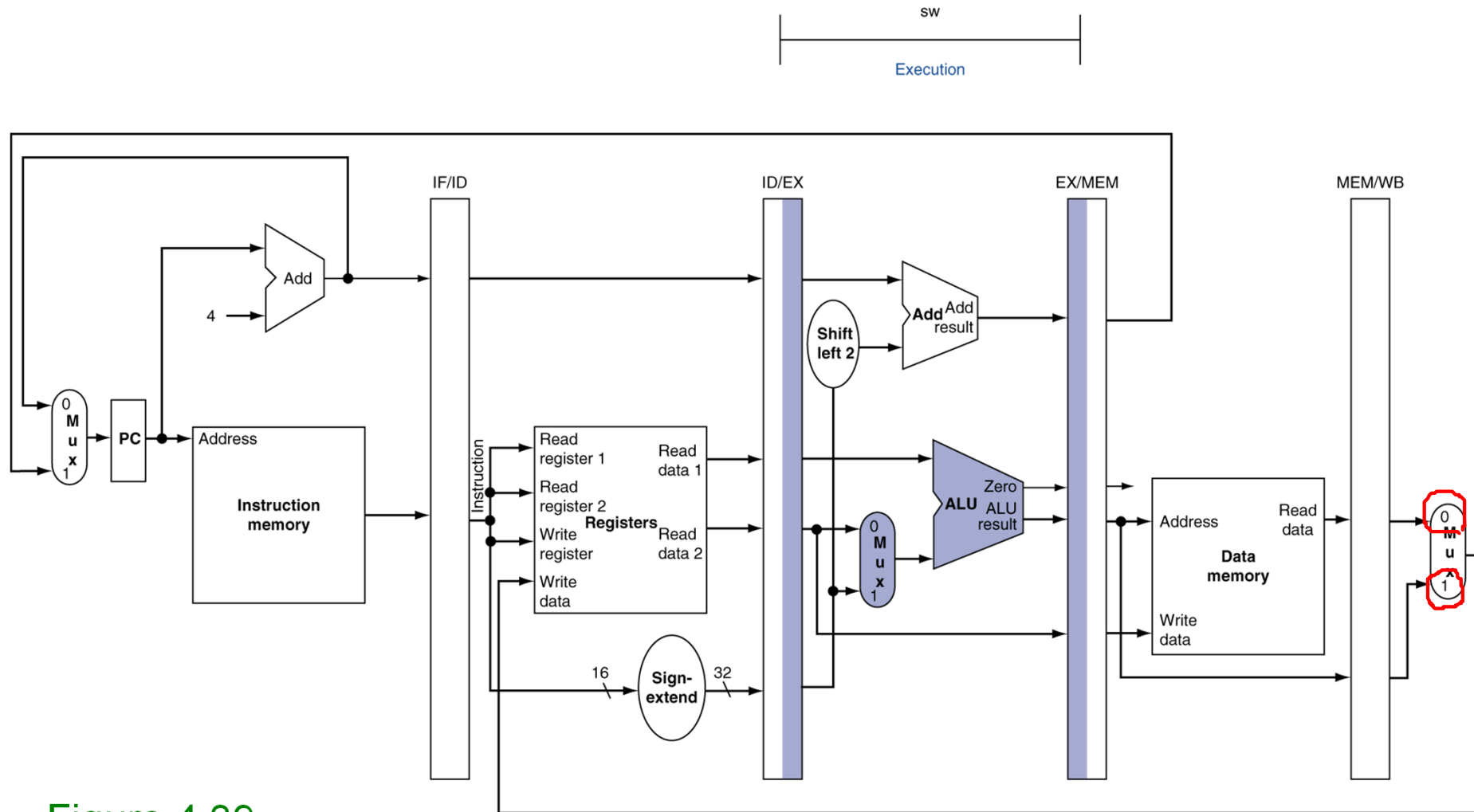


Figure 4.39

sw Instruction in MEM Stage

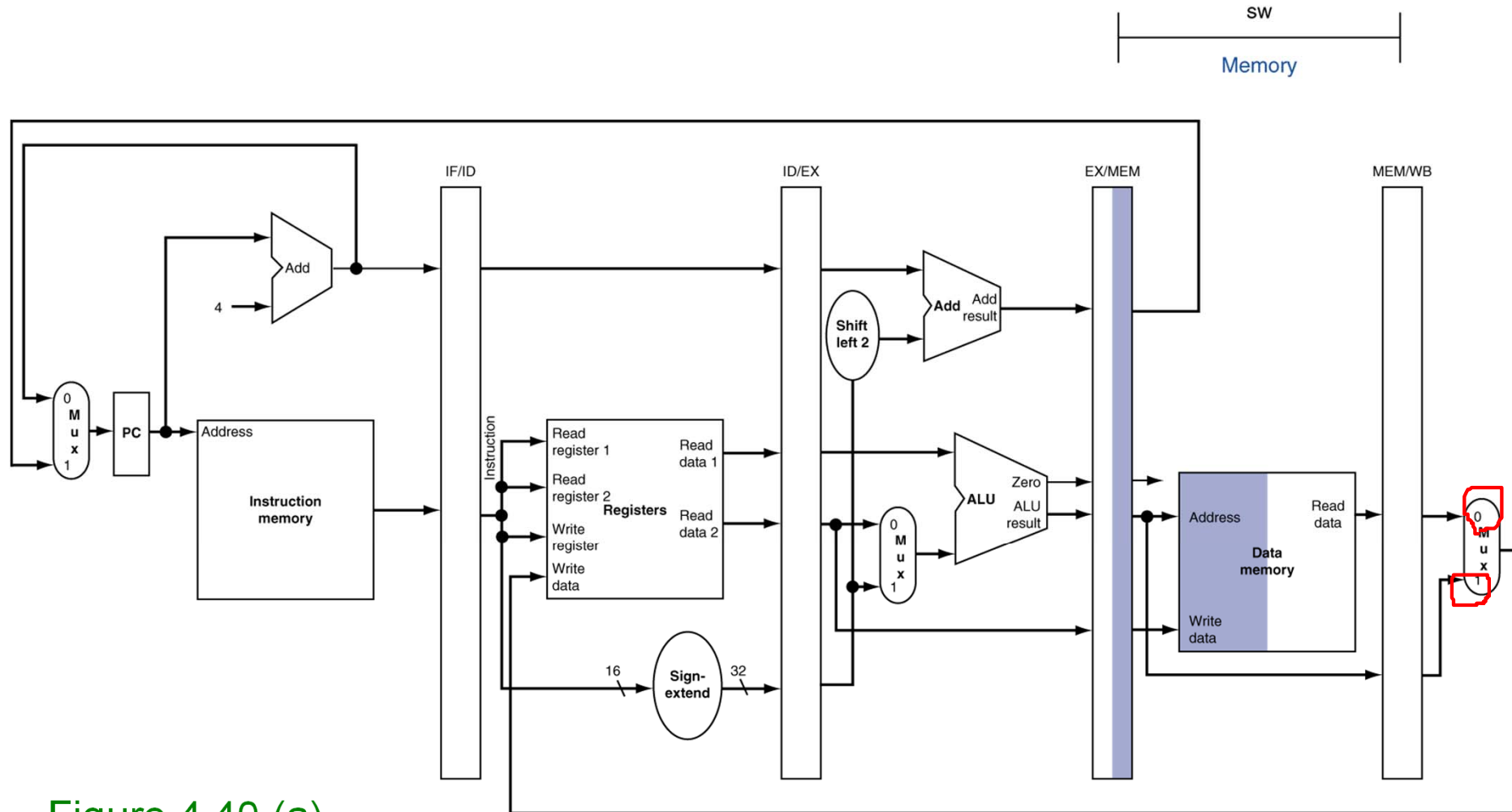


Figure 4.40 (a)

sw Instruction in WB Stage

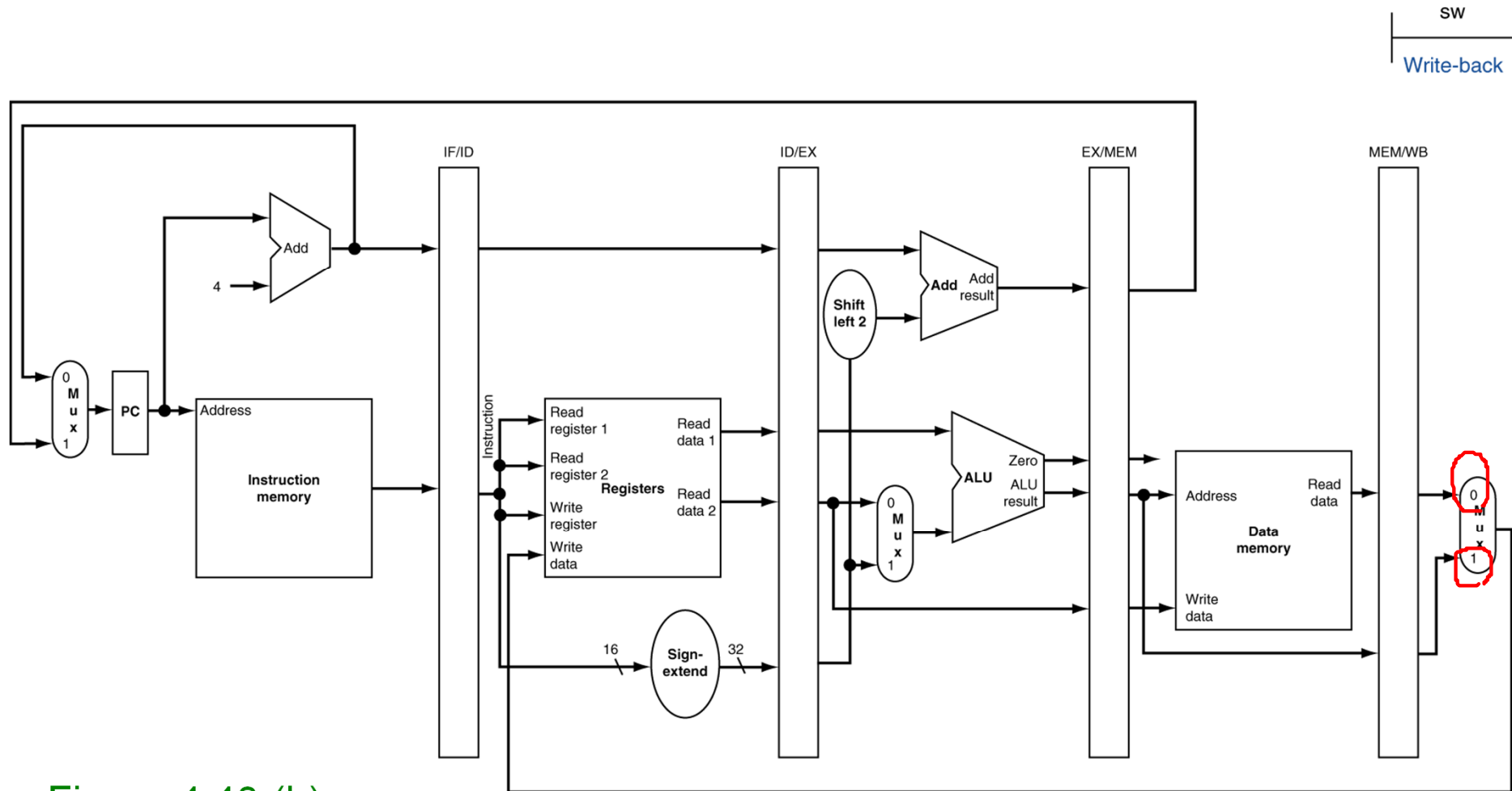


Figure 4.40 (b)

Pipelined Control

- Pipelined datapath with control signals

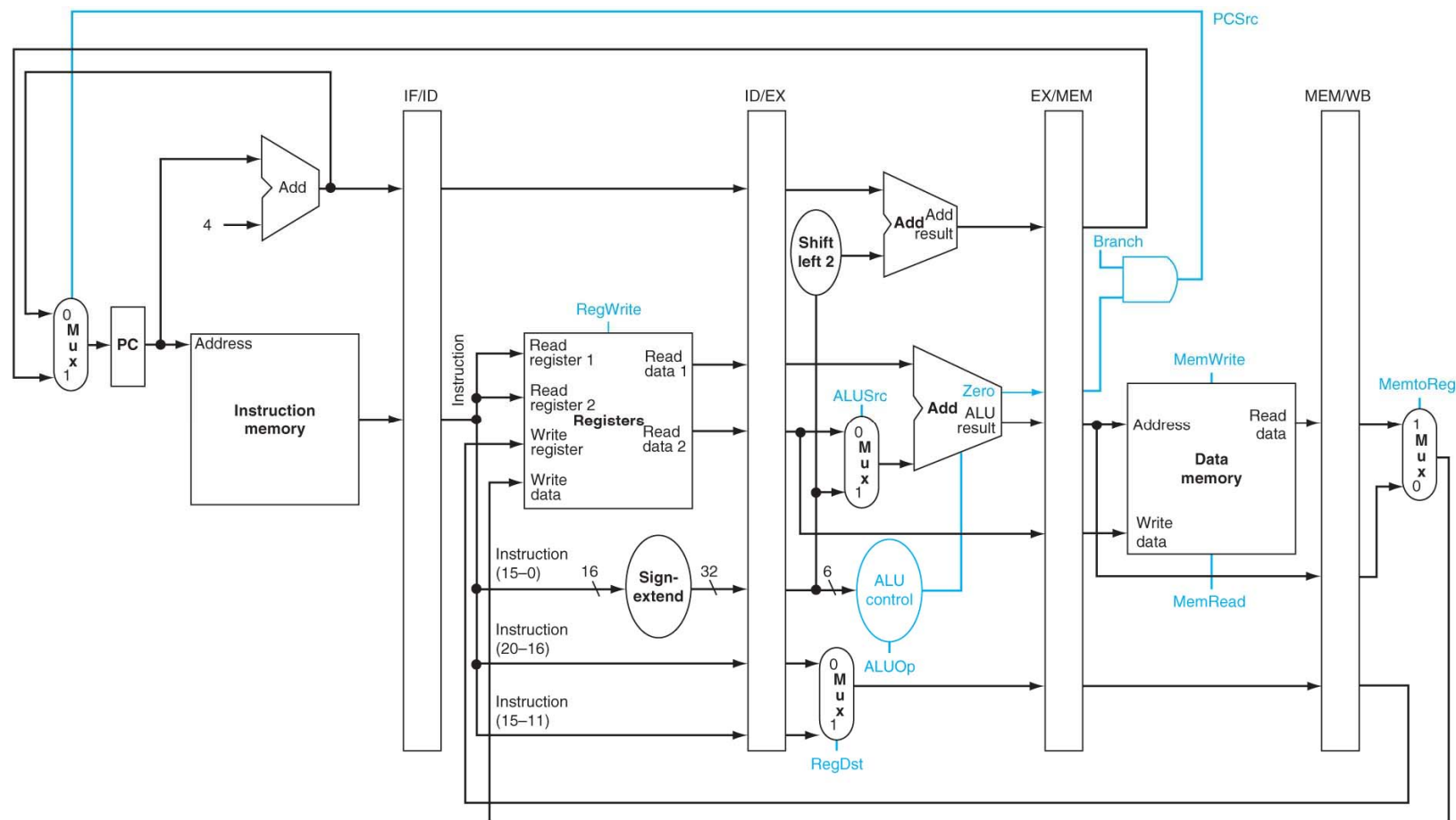


Figure 4.46

Control Signals

1. IF : nothing (the same thing happens at every clock cycle)
2. ID : nothing
3. EX : RegDst, ALUOp, ALUSrc
4. MEM : Branch(for beq), MemRead(for lw), MemWrite(for sw)
5. WB : MemtoReg, RegWrite

Instruction	EX stage control lines				MEM stage control lines			Write back stage control lines	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Branch	Mem Read	Mem Write	Reg Write	Memto-Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

Figure 4.49

Control Signals for Each Stage

- Control signals derived from instruction

 


Figure 4.50

Complete Pipelined Datapath

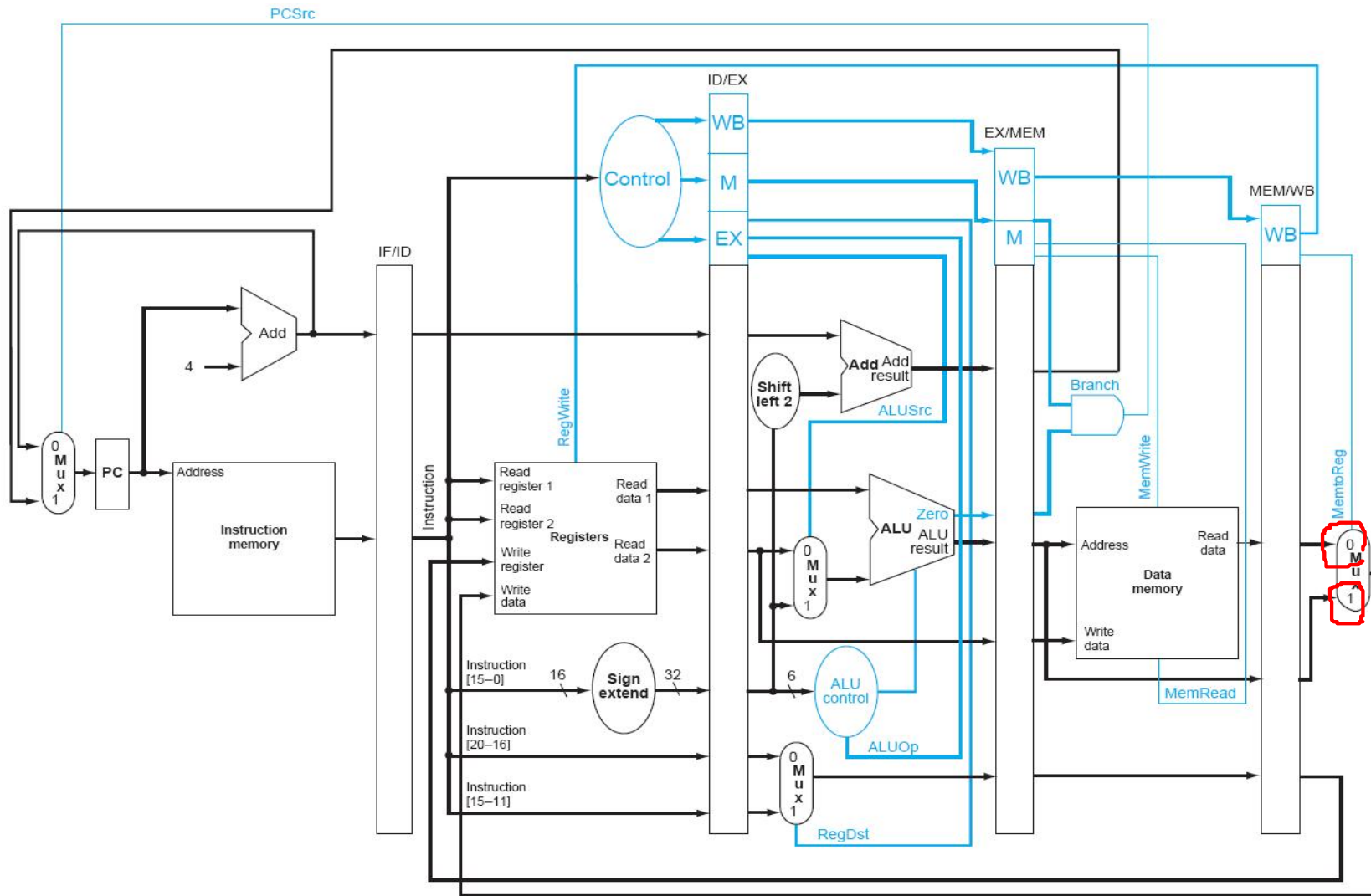



Figure 4.51

Complete Pipelined Datapath

```

1000: lw $1, 81($2)
1004: add $3,$4,$5
1008: sub $6,$7,$8
1012: slt $9,$10,$11
1016: beq $12,$13, XX
    
```

$\$r = r+1$
 $M[x] = x*2$

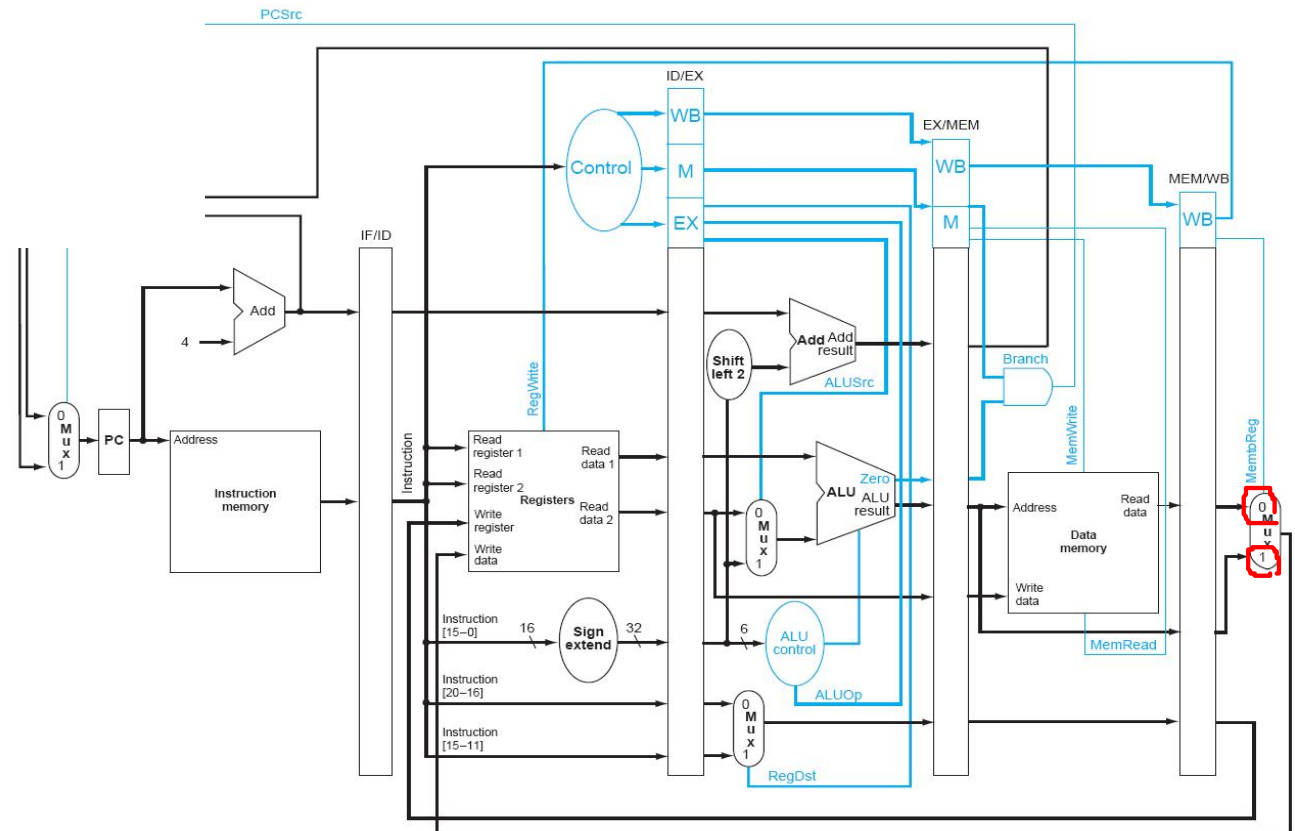

Structural Hazards

- Conflict for use of a resource
- In MIPS pipeline with a single memory
 - ❖ Load/store requires data access
 - ❖ Instruction fetch would have to **stall** for that cycle
 - ◆ Would cause a pipeline “bubble”
- Hence, pipelined datapaths require separate instruction/data memories
 - ❖ Or separate instruction/data caches